
# **Arduino Board Setup**

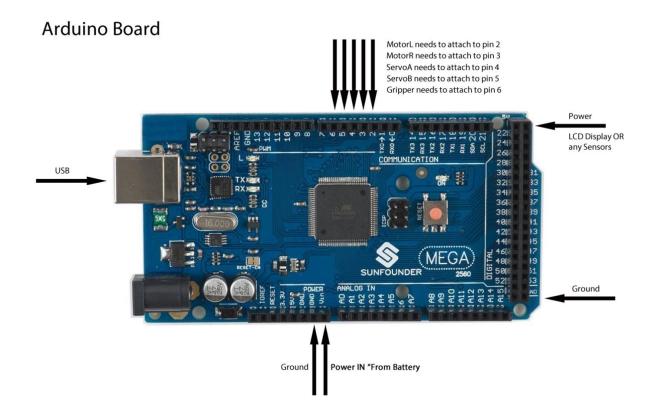

## **NOTE:** Make sure battery switch is OFF.

### Step 1

- Connect red battery wire/connector to positive side of strip.
- Connect black battery wire/connector to negative side of strip.





- Connect all black (negative) servo wires to negative side of strip.
- Connect all red (positive/middle wire) positive side of strip.

#### Step 3

• Connect all servo signal wire (yellow) to correct pin on arduino. See picture at top for correct pin location. Repeat for all servos remaining...

### Step 4

• Connect a red wire/connector from positive side of strip to Vin. See picture at top for correct pin location.

Connect a black wire/connector from negative side of strip to GND. See picture at top for correct pin location.

